




Key No. 60

 Seat Number

**King Mongkut's University of Technology Thonburi
 Midterm Examination
 Semester 1 -- Academic Year 2017**

Subject: EIE 210 Electronic Devices and Circuit Design I

For: Electrical Communication and Electronic Engineering, 2nd Yr (Inter. Program)

Exam Date: Wednesday September 27, 2017

Time: 13.00-16.00 pm.

Instructions:-

1. This exam consists of 5 problems with a total of 8 pages, including the cover.
2. This exam is closed books.
3. You are **not** allowed to use any written A4 note for this exam.
4. Answer each problem on the exam itself.
5. A calculator compiling with the university rule is allowed.
6. A dictionary is **not** allowed.
7. **Do not** bring any exam papers and answer sheets outside the exam room.
8. Open Minds ... No Cheating! GOOD LUCK!!!

Remarks:-


- **Raise your hand when you finish the exam to ask for a permission to leave the exam room.**
- **Students who fail to follow the exam instruction might eventually result in a failure of the class or may receive the highest punishment with university rules.**
- **Carefully read the entire exam before you start to solve problems. Before jumping into the mathematics, think about what the question is asking. Investing a few minutes of thought may allow you to avoid twenty minutes of needless calculation!**

| Exam No. | 1 | 2 | 3 | 4 | 5 | 6 | 7 | 8 | TOTAL |
|--------------|-----------|-----------|-----------|-----------|-----------|---|---|---|-----------|
| Full Score | <u>10</u> | <u>10</u> | <u>20</u> | <u>30</u> | <u>10</u> | | | | <u>80</u> |
| Graded Score | | | | | | | | | |

Name _____ Student ID _____

This examination is designed by
 Asst. Prof. Kamon Jirasereamornkul. Ph.D, & Prof. Niel S. Kurt. Ph.D.; Tel: 9067.

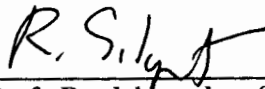This examination has been approved by the committees of the ENE department.



 (Assoc. Prof. Rardchawadee Silapunt, Ph.D.)
 Head of Electronic and Telecommunication Engineering Department

1. A pn-junction silicon diode ($T = 350 \text{ K}$) is doped with the following concentrations: $N_A = 2.5 \times 10^{16} \text{ cm}^{-3}$, $N_D = 4.5 \times 10^{13} \text{ cm}^{-3}$. Calculate the intrinsic carrier density n_i of silicon and the junction built-in voltage V_0 (10 marks).

2. Analyze and draw the output of the clipper in Figure 1. Assume that the diode is an ideal one (10 marks).

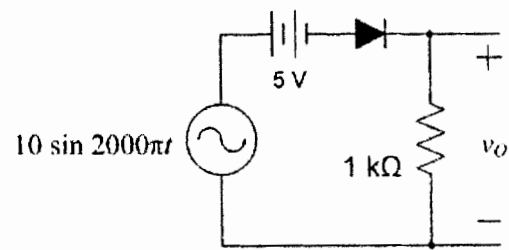


Fig. 1

3. Consider the circuit in Figure 2. Sketch the waveform of output voltage v_o and current i_o compare with secondary voltage v_s . Also, determine the peak values of i_o and the reverse voltage at D_1 . (20 marks)


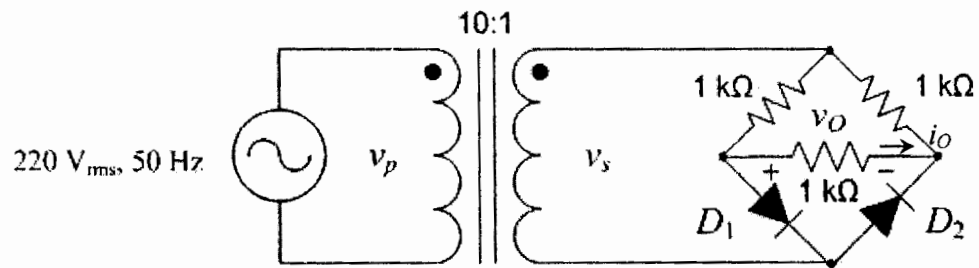


Fig. 2

4. A zener diode whose nominal voltage is 6.8 V at 20 mA is used in the design of a shunt regulator fed from a 24-V supply. The knee current I_{ZK} is specified to be 5 mA. The load current varies over a range of 0 mA to 200 mA.
- 4.1) Draw a sketch of the circuit (input voltage, zener diode, shunt resistor R_S , and load R_L) (10 marks).
 - 4.2) Find a suitable value for the shunt resistor R_S (10 marks).
 - 4.3) Calculate the maximum power dissipation of the zener diode and of the shunt resistor R_S (10 marks)?

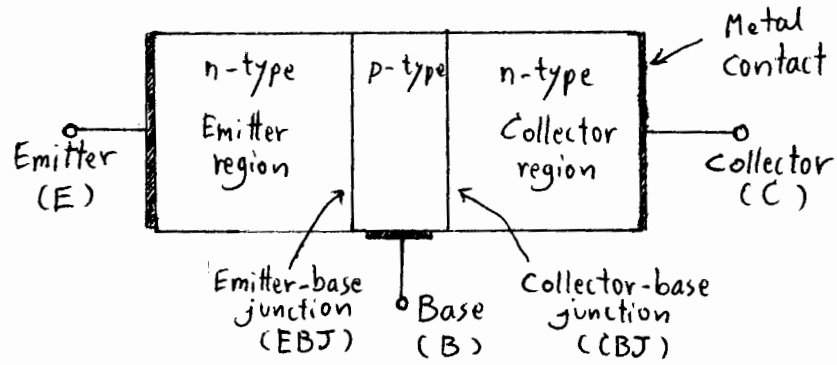5. Bipolar junction transistor in npn-format and in active mode: Check the answers for the following questions (10 marks):



| | | | |
|---|-----------------------------------|-----------------------------------|--|
| The emitter-base junction is in forward bias | <input type="checkbox"/> yes | <input type="checkbox"/> no | |
| The collector-base junction is in forward bias | <input type="checkbox"/> yes | <input type="checkbox"/> no | |
| The collector current depends on the collector-base voltage | <input type="checkbox"/> yes | <input type="checkbox"/> no | |
| The collector current depends on the emitter-base voltage | <input type="checkbox"/> yes | <input type="checkbox"/> no | |
| The common-emitter current gain β is in the range of | <input type="checkbox"/> 0.1 - 10 | <input type="checkbox"/> 50 - 200 | <input type="checkbox"/> $10^5 - 10^7$ |

Summary of given formulars

| Table 1.3 Summary of Important Semiconductor Equations | | |
|---|---|--|
| Quantity | Relationship | Values of Constants and Parameters (for Intrinsic Si at $T = 300\text{ K}$) |
| Carrier concentration in intrinsic silicon (cm^{-3}) | $n_i = BT^{-3/2} e^{-E_g/2kT}$ | $B = 7.3 \times 10^{15} \text{ cm}^{-3} \text{ K}^{-3/2}$ $E_g = 1.12 \text{ eV}$ $k = 8.62 \times 10^{-5} \text{ eV/K}$ $n_i = 1.5 \times 10^{10} / \text{cm}^3$ |
| Diffusion current density (A/cm^2) | $J_p = -qD_p \frac{dp}{dx}$ $J_n = qD_n \frac{dn}{dx}$ | $q = 1.60 \times 10^{-19} \text{ coulomb}$ $D_p = 12 \text{ cm}^2/\text{s}$ $D_n = 34 \text{ cm}^2/\text{s}$ |
| Drift current density (A/cm^2) | $J_{\text{drift}} = q(p\mu_p + n\mu_n)E$ | $\mu_p = 480 \text{ cm}^2/\text{V} \cdot \text{s}$ $\mu_n = 1350 \text{ cm}^2/\text{V} \cdot \text{s}$ |
| Resistivity ($\Omega \cdot \text{cm}$) | $\rho = 1/[q(p\mu_p + n\mu_n)]$ | μ_p and μ_n decrease with the increase in doping concentration |
| Relationship between mobility and diffusivity | $\frac{D_p}{\mu_p} = \frac{D_n}{\mu_n} = V_T$ | $V_T = kT/q \approx 25.9 \text{ mV}$ |
| Carrier concentration in n-type silicon (cm^{-3}) | $n_{n0} \approx N_D$ $p_{n0} = n_i^2/N_D$ | |
| Carrier concentration in p-type silicon (cm^{-3}) | $p_{p0} \approx N_A$ $n_{p0} = n_i^2/N_A$ | |
| Junction built-in voltage (V) | $V_0 = V_T \ln\left(\frac{N_A N_D}{n_i^2}\right)$ | |
| Width of depletion region (cm) | $\frac{x_n}{x_p} = \frac{N_A}{N_D}$ $W = x_n + x_p$ $= \sqrt{\frac{2\epsilon_s}{q} \left(\frac{1}{N_A} + \frac{1}{N_D}\right) (V_0 + V_R)}$ | $\epsilon_s = 11.7\epsilon_0$ $\epsilon_0 = 8.854 \times 10^{-14} \text{ F/cm}$ |

| Table 1.3 continued | | |
|--|---|---|
| Quantity | Relationship | Values of Constants and Parameters (for Intrinsic Si at $T = 300$ K) |
| Charge stored in depletion layer (coulomb) | $Q_j = q \frac{N_A N_D}{N_A + N_D} AW$ | |
| Forward current (A) | $I = I_p + I_n$ $I_p = Aq n_i^2 \frac{D_p}{L_p N_D} (e^{v/V_T} - 1)$ $I_n = Aq n_i^2 \frac{D_n}{L_n N_A} (e^{v/V_T} - 1)$ | |
| Saturation current (A) | $I_s = Aq n_i^2 \left(\frac{D_p}{L_p N_D} + \frac{D_n}{L_n N_A} \right)$ | |
| I - V relationship | $I = I_s (e^{v/V_T} - 1)$ | |
| Minority-carrier lifetime (s) | $\tau_p = L_p^2/D_p$ $\tau_n = L_n^2/D_n$ | $L_p, L_n = 1 \mu\text{m to } 100 \mu\text{m}$ $\tau_p, \tau_n = 1 \text{ ns to } 10^4 \text{ ns}$ |
| Minority-carrier charge storage (coulomb) | $Q_p = \tau_p I_p$ $Q_n = \tau_n I_n$ $Q = Q_p + Q_n = \tau_T I$ | |
| Depletion capacitance (F) | $C_{j0} = A \sqrt{\left(\frac{\epsilon_s q}{2}\right) \left(\frac{N_A N_D}{N_A + N_D}\right) \frac{1}{V_0}}$ $C_j = C_{j0} / \left(1 + \frac{V_R}{V_0}\right)^m$ | $m = \frac{1}{3} \text{ to } \frac{1}{2}$ |
| Diffusion capacitance (F) | $C_d = \left(\frac{\tau_T}{V_T}\right) I$ | |