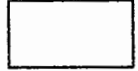




เลขที่ห้องสอบ



มหาวิทยาลัยเทคโนโลยีพระจอมเกล้าธนบุรี
ข้อสอบกลางภาคการศึกษาที่ 1/2561

วันศุกร์ที่ 5 ตุลาคม 2561

เวลา 13.00 -16.00 น.

วิชา CPE 223 Digital Electronics and Logic Design

น.ศ. วิศวกรรมคอมพิวเตอร์

คำสั่ง

1. ข้อสอบมีทั้งหมด 8 ข้อ จำนวน 10 แผ่น (รวมแผ่นนี้) คะแนนรวม 30 คะแนน
2. ให้นักศึกษาทำข้อสอบทุกข้อลงในช่องว่างที่เตรียมไว้ให้ ในตัวข้อสอบชุดนี้
3. ไม่อนุญาตให้ใช้เครื่องคำนวณ
4. ไม่อนุญาตให้นำเอกสารใดๆ เข้าห้องสอบ
5. เขียนชื่อ และ รหัสประจำตัว ลงในปกหน้าฉบับนี้

ผศ.สนั่น สระแก้ว

ผู้ออกข้อสอบ

0-2470-9083

ข้อสอบนี้ได้ผ่านการประเมินจากภาควิชาวิศวกรรมคอมพิวเตอร์แล้ว

รศ.ดร.พีรพล ศิริพงษ์วุฒิกร

ประธานหลักสูตร

ข้อ	1	2	3	4	5	6	7	8	รวม
คะแนนเต็ม	3	2	3	4	4	4	6	4	30
คะแนนที่ได้									

ชื่อ รหัสประจำตัว.....

1. Use 16-bit 2's complement binary to represent the following decimal numbers: (3 points)

a) 14,320

b) -12,035

c) 0.12

2. Perform binary additions or subtractions and determine whether the overflow occurs.

(2 points)

$$\begin{array}{r} \text{a) } 1001\ 1011 \\ \quad \quad \quad + \\ \hline 1011\ 0110 \end{array}$$

$$\begin{array}{r} \text{b) } 0110\ 1010 \\ \quad \quad \quad - \\ \hline 1010\ 1111 \end{array}$$

$$\begin{array}{r} \text{c) } 1000\ 0001 \\ \quad \quad \quad - \\ \hline 1011\ 0110 \end{array}$$

$$\begin{array}{r} \text{d) } 0110\ 1010 \\ \quad \quad \quad + \\ \hline 0100\ 0101 \end{array}$$

3. Simplify the following Boolean functions:

(3 points)

a) $F(A,B,C,D) = \Sigma (0,1,4,5,12,13)$

b) $F(W,X,Y,Z) = \Sigma (1,7,11,13) + d(0,5,10,15)$

c) $F(A,B,C,D) = ABC + BCD + ACD + ABD$

4. Given the following function in sum of products form

(4 points)

$$F(A,B,C,D) = \overline{A}BC + AD + AC$$



a) Determine \overline{F} in minimized sum of products form.

b) Implement \overline{F} using NAND gates only.

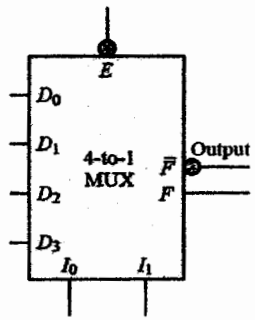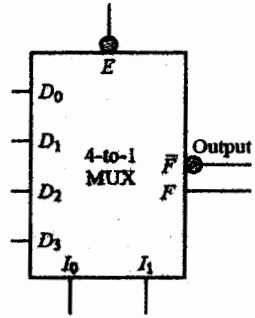5. Implement the following Boolean function using two 4-to-1 multiplexers.

(4 points)

$$F(A,B,C,D) = \Sigma (2,4,6,9,10,11,15)$$



6. A combinational circuit is specified by the following three Boolean functions:



$$F_1(A,B,C) = \Sigma (0,3,4)$$

$$F_2(A,B,C) = \Sigma (1,2,7)$$


$$F_3(A,B,C) = \Pi (0,1,2,4)$$

Implement the circuit with two 2-to-4 decoders.


(4 points)

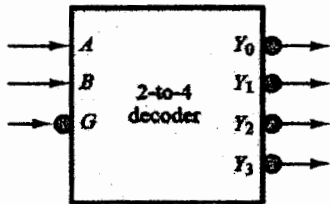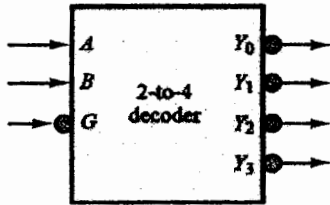

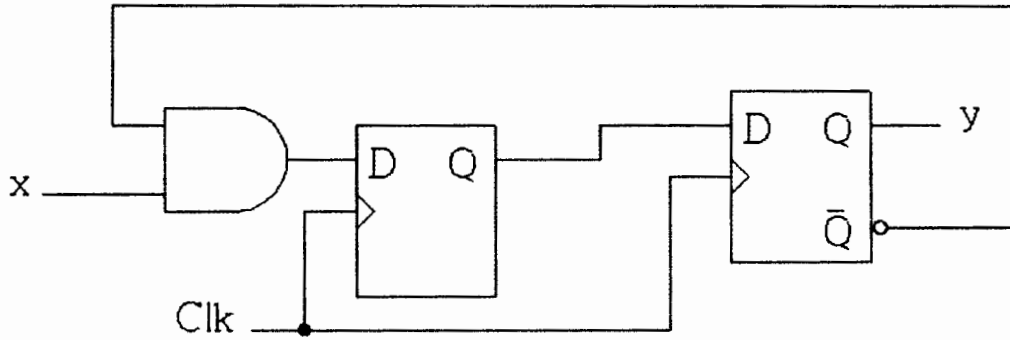7. Given the circuit shown below(Assume flip-flops are initially in reset state): (6 points)




a) Determine the output (y) waveform

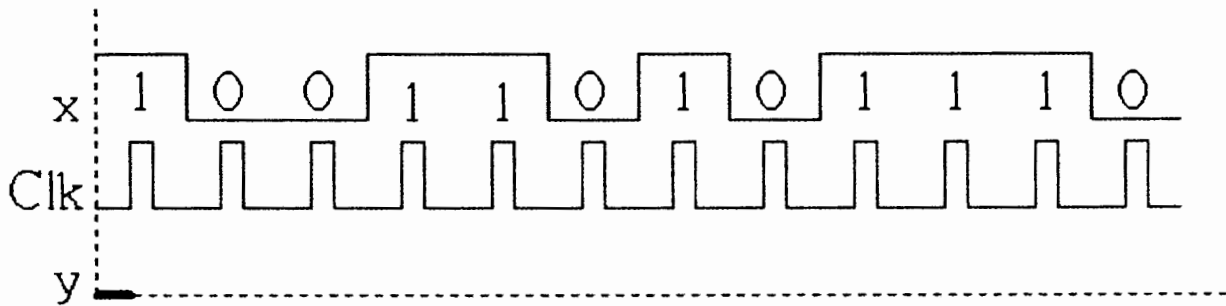

b) Sketch the state diagram

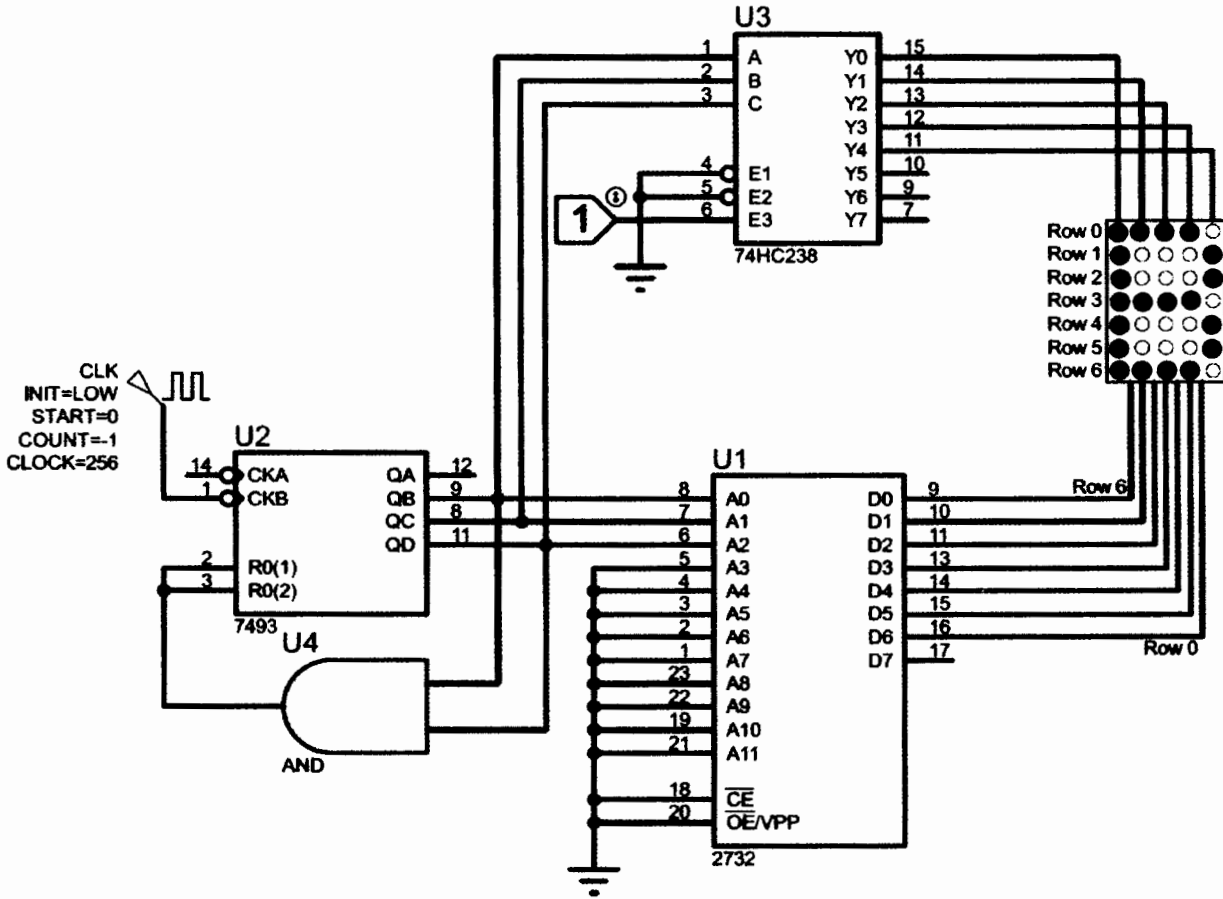8. Given the circuit below(Similar to the one in the Laboratory section):



Specify the ROM contents so that the dot-matrix displays the letter “B” as shown: (4 points)

Address (in binary)	ROM contents (in binary)
0000	
0001	
0010	
0011	
0100	
0101	
0110	
0111	

Supplemental

Table 2.1
Postulates and Theorems of Boolean Algebra

Postulate 2	(a)	$x + 0 = x$	(b)	$x \cdot 1 = x$
Postulate 5	(a)	$x + x' = 1$	(b)	$x \cdot x' = 0$
Theorem 1	(a)	$x + x = x$	(b)	$x \cdot x = x$
Theorem 2	(a)	$x + 1 = 1$	(b)	$x \cdot 0 = 0$
Theorem 3, involution		$(x')' = x$		
Postulate 3, commutative	(a)	$x + y = y + x$	(b)	$xy = yx$
Theorem 4, associative	(a)	$x + (y + z) = (x + y) + z$	(b)	$x(yz) = (xy)z$
Postulate 4, distributive	(a)	$x(y + z) = xy + xz$	(b)	$x + yz = (x + y)(x + z)$
Theorem 5, DeMorgan	(a)	$(x + y)' = x'y'$	(b)	$(xy)' = x' + y'$
Theorem 6, absorption	(a)	$x + xy = x$	(b)	$x(x + y) = x$

Table 5.1
Flip-Flop Characteristic Tables

JK Flip-Flop			
J	K	Q(t + 1)	
0	0	Q(t)	No change
0	1	0	Reset
1	0	1	Set
1	1	Q'(t)	Complement

D Flip-Flop		
D	Q(t + 1)	
0	0	Reset
1	1	Set

T Flip-Flop		
T	Q(t + 1)	
0	Q(t)	No change
1	Q'(t)	Complement